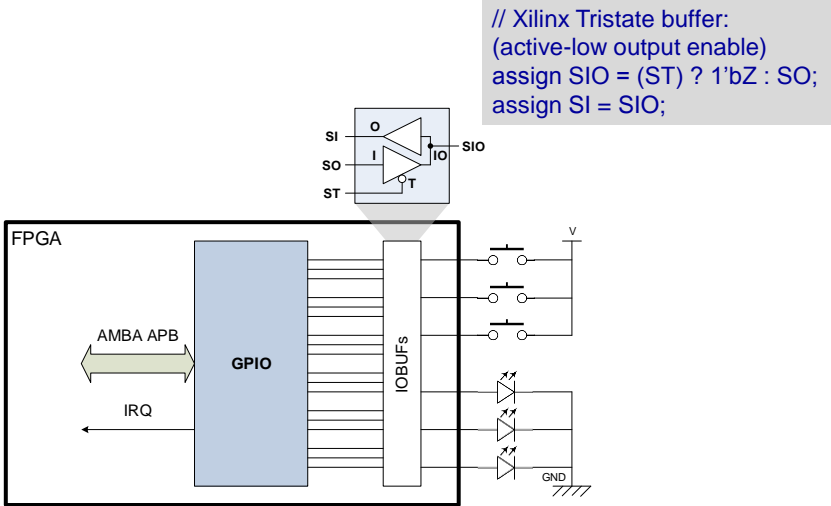


# GPIO with AMBA APB interface


2020

Ando Ki  
(adki@future-ds.com)

## GPIO testing environment




## Pushbutton switch and LED

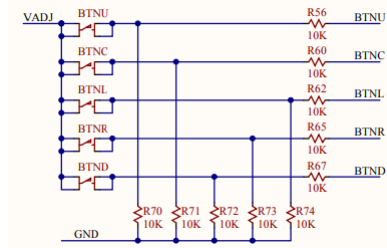

```
set_property PACKAGE_PIN P16 [get_ports {BTNC}]; # "BTNC"
set_property PACKAGE_PIN R16 [get_ports {BTND}]; # "BTND"
set_property PACKAGE_PIN N15 [get_ports {BTNL}]; # "BTNL"
set_property PACKAGE_PIN R18 [get_ports {BTNR}]; # "BTNR"
set_property PACKAGE_PIN T18 [get_ports {BTNU}]; # "BTNU"
set_property IOSTANDARD LVCMOS25 [get_ports BTN?]
```



VADJ selecting jump

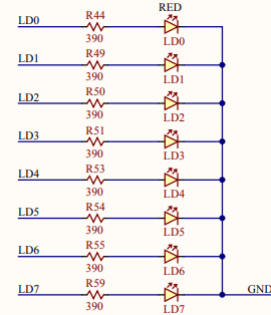

```
set_property PACKAGE_PIN T22 [get_ports {LD0}]; # "LD0"
set_property PACKAGE_PIN T21 [get_ports {LD1}]; # "LD1"
set_property PACKAGE_PIN U22 [get_ports {LD2}]; # "LD2"
set_property PACKAGE_PIN U21 [get_ports {LD3}]; # "LD3"
set_property PACKAGE_PIN V22 [get_ports {LD4}]; # "LD4"
set_property PACKAGE_PIN W22 [get_ports {LD5}]; # "LD5"
set_property PACKAGE_PIN U19 [get_ports {LD6}]; # "LD6"
set_property PACKAGE_PIN U14 [get_ports {LD7}]; # "LD7"
set_property IOSTANDARD LVCMOS33 [get_ports LD?]
```

Copyright © 2020 by Ando Ki

GPIO ( 3 )

## GPIO

### General Purpose Input/Output

- ◆ an uncommitted digital signal pin on an integrated circuit or electronic circuit board whose behavior—including whether it acts as input or output—is controllable by the user at run time.

### Capabilities of GPIO

- ◆ GPIO pins can be configured to be input or output
- ◆ GPIO pins can be enabled/disabled
- ◆ Input values are readable (typically high or low)
- ◆ Output values are writable/readable
- ◆ Input values can often be used as IRQs

Copyright © 2020 by Ando Ki

GPIO ( 4 )

## Requirements

- It support AMBA APB.
- The number of GPIO ports or pins can be defined when it is instantiated.
  - ◆ Up to 32
  - ◆ Need parameterized design
- Each pin can be input or output by control register
  - ◆ Output port can be read as well
- Input pins can be used as interrupt
  - ◆ It can be edge sensitive for both rising and falling.
  - ◆ It can be level sensitive for both high and low.

## GPIO module



### ■ Module

```
module gpio_apb #(parameter GPIO_WIDTH=32)
(
    input  wire          PRESETn
    , input  wire          PCLK
    , input  wire          PSEL
    , input  wire          PENABLE
    , input  wire [31:0]    PADDR
    , input  wire          PWRITE
    , output reg [31:0]     PRDATA
    , input  wire [31:0]    PWDATA
    , input  wire [GPIO_WIDTH-1:0] GPIO_I
    , output wire [GPIO_WIDTH-1:0] GPIO_O
    , output wire [GPIO_WIDTH-1:0] GPIO_T
    , output wire          IRQ
);
.....
endmodule
```

## GPIO registers: CSR (Control Status Register)
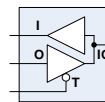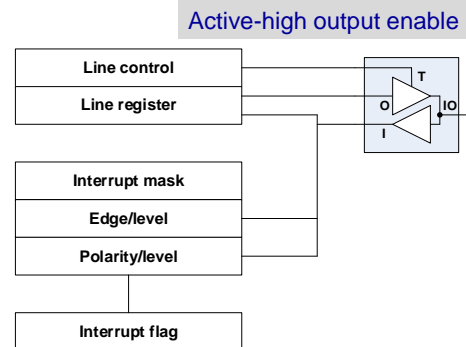
### [REGISTERS]

- ◆ 0x00: Line Control Register
  - '0' = input mode (default)
  - '1' = output mode
- ◆ 0x04: Line Register
  - Current GPIO pin level
- ◆ 0x08: Interrupt Mask Register
  - '0' = enabled
  - '1' = masked (disabled) (default)
- ◆ 0x0C: Interrupt Flag
  - '0' = no interrupt
  - '1' = interrupt
- ◆ 0x10: Interrupt Edge/Level Sensitivity Mode Register
  - '0' = Level sensitivity mode (default)
  - '1' = Edge sensitivity mode
- ◆ 0x14: Interrupt Pol Sensitivity Mode Register
  - '0' = active-low for level mode, falling for edge mode (default)
  - '1' = active-high for level mode, rising for edge mode



// Xilinx Tristate buffer:  
assign SIO = (ST) ? 1'bZ : SO;  
assign SI = SIO;

Copyright © 2020 by Ando Ki

GPIO (7)

## How GPIO works

### ■ Use a pin as an input:

- ◆ Program the corresponding bit in the Control Register to 'input mode' ('0'). Then, the pin's state (input level) can be checked by reading the Line Register.
  - Note that writing to the GPIO pin's Line Register bit while in input mode has no effect.

### ■ Use a pin as an output:

- ◆ Program the corresponding bit in the Control Register to 'output mode' ('1'). Then, program the GPIO pin's output level by writing to the corresponding bit in the Line Register.
  - Note reading the GPIO pin's Line Register bit while in output mode returns the current input pin level so that it may not reflect the value written.

### ■ Use a pin as an interrupt source:

- ◆ Program the corresponding bit in the Edge Register to the desired sensitivity mode (level or edge). Program the corresponding bit in the Pol Register to the desired sensitivity mode (low/falling or high/rising). Program the corresponding bit in the Mask Register to 'un-masked mode' ('0').


Copyright © 2020 by Ando Ki

GPIO (8)

## What to do for IP

Make your own project to build GPIO IP itself.

◆ ex\_gpio\_apb

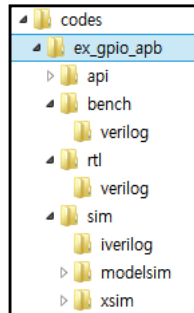


Copyright © 2020 by Ando Ki

BRAM (9)
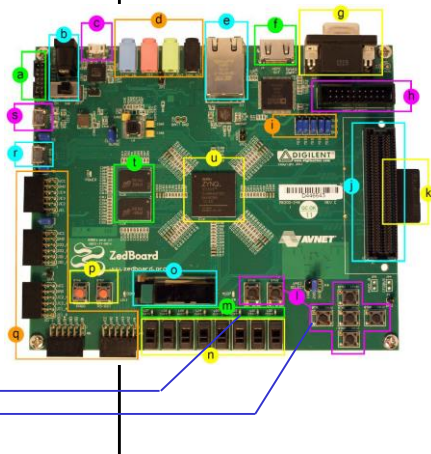
## Top level design for ZedBoard

fpga.v (i.e., fpga\_zed.v)

```
module fpga #(parameter SL_PCLK_FREQ    =80_000_000
                    , USR_CLK_FREQ    =80_000_000 )
(
    input  wire    BOARD_RST_SW
    , input  wire    BOARD_CLK_IN
    , input  wire    SL_RST_N
    , output wire    SL_CS_N
    , output wire    SL_PCLK
    , input  wire    SL_FLAGA
    , input  wire    SL_FLAGB
    , input  wire    SL_FLAGC
    , input  wire    SL_FLAGD
    , output wire    SL_RD_N
    , output wire    SL_WR_N
    , output wire    SL_OE_N
    , output wire    SL_PKTEND_N
    , output wire    [ 1:0] SL_AD
    , inout  wire    [31:0] SL_DT
    , input  wire    [ 1:0] SL_MODE
    , inout  wire    LD0
    , inout  wire    LD1
    , inout  wire    LD2
    , inout  wire    LD3
    , inout  wire    BTNU
    , inout  wire    BTNL
    , inout  wire    BTNR
    , inout  wire    BTND
);
```




Copyright © 2020 by Ando Ki

GPIO (10)
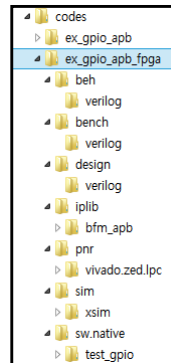
## What to do for FPGA board

After preparing your own 'gpio\_apb.v', make FPGA project which uses push-button switches and LED's.

- ◆ Pushbutton X corresponds to LED X.
- ◆ Pushing a pushbutton switch alternately toggles its corresponding LED light on OR off.
  - It may not work correctly due to bouncing problem.
  - Do not try to push the BTN-C, which is system reset.




Copyright © 2020 by Ando Ki

BRAM ( 11 )
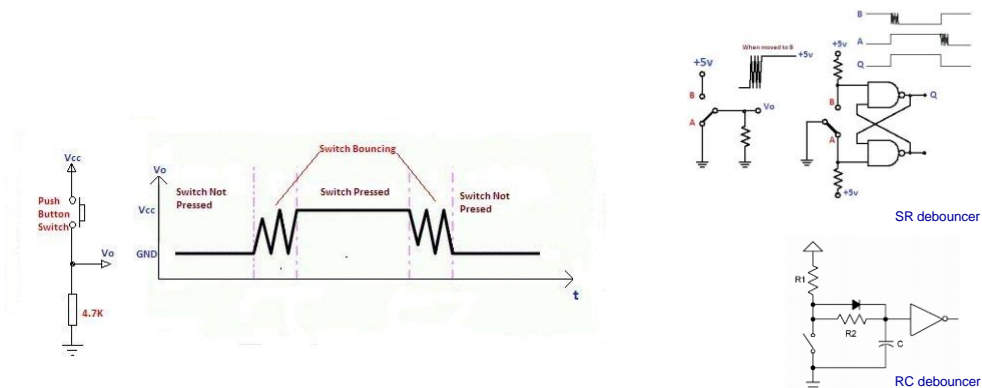
## How to deal with bounce

- Bouncing is the tendency of any two metal contacts in an electronic device to generate multiple signals as the contacts close or open
- De-bouncing is any kind of hardware device or software that ensures that only a single signal will be acted upon for a single opening or closing of a contact.



Copyright © 2020 by Ando Ki

GPIO ( 12 )